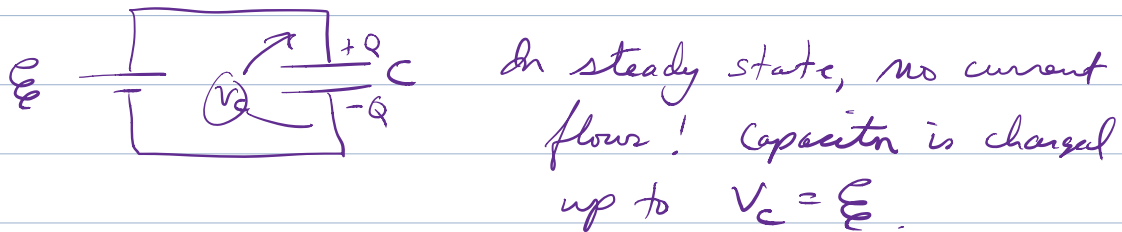


## 23.6 capacitors in series and parallel

Capacitor circuit symbol:  $-|$  reminds us of the parallel plates.


Basic capacitor circuit:




$$\text{Recall } Q = C (\Delta V)$$

$$Q = C \mathcal{E}$$

Parallel Combination

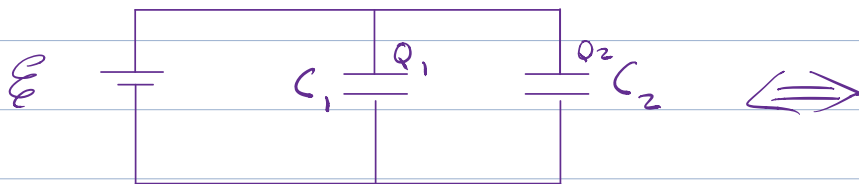

What is the net effective capacitance?

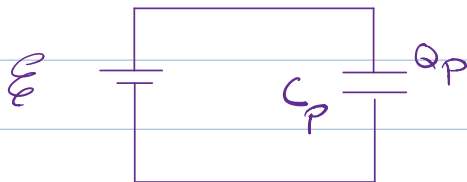

The total charge stored is  $Q_p = Q_1 + Q_2$   
Use the relation  $Q = C(\Delta V)$ , while recognizing  $\Delta V = \mathcal{E}$  for both capacitors.


$$Q_p = Q_1 + Q_2$$

$$C_p \mathcal{E} = C_1 \mathcal{E} + C_2 \mathcal{E}$$

$$\therefore \boxed{C_p = C_1 + C_2}$$

recall for parallel plates:  $C = \frac{\epsilon_0 A}{d}$ . we have essentially added more area.

Series combination:

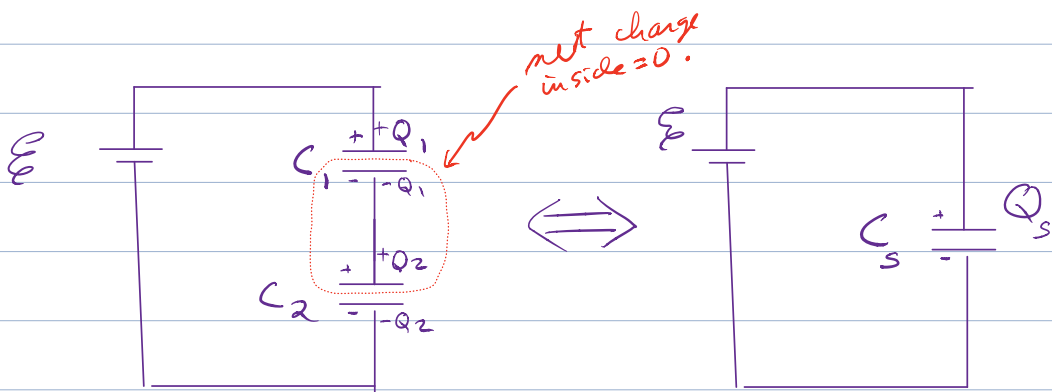

$$\therefore Q_1 = Q_2 = Q_s$$

$$\text{KVL: } \mathcal{E} - \Delta V_1 - \Delta V_2 = 0$$

$$\frac{Q_s}{C_s} - \frac{Q_1}{C_1} - \frac{Q_2}{C_2} = 0$$

$$\boxed{\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2}}$$

$$Q_s = C_s \mathcal{E}$$

$$\Rightarrow \mathcal{E} = \frac{Q_s}{C_s}$$

series equivalent.

$$C = \frac{\epsilon_0 A}{d}, \text{ as if we}$$

combined distances.


## 23.7 RC Circuits

Important application = timing.

Units note


$$[RC] = \Omega \cdot F = \frac{V}{A} \cdot \frac{C}{V} = \frac{1}{A} \cdot C = \text{seconds}.$$

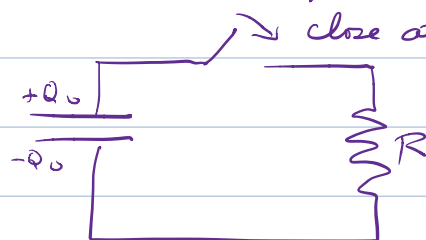Discharge: consider a capacitor initially charged to voltage  $V_0$ , with charge  $Q_0 = CV_0$ .




Let  $q$  = charge at any instant.

initially

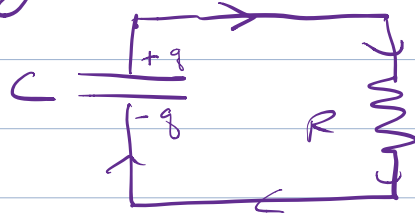

current flows as charges leave + plate.

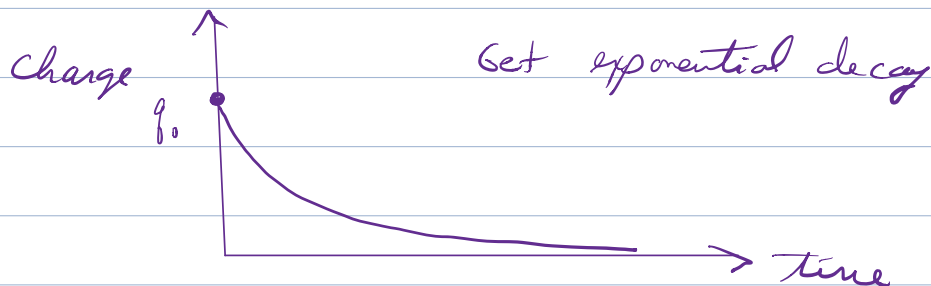But ... as charges leave,  $\Delta V = q/C$  decreases, so the voltage across the resistor decreases and  $i$  decreases.




$$q = Q_0 e^{-t/RC}$$

$$q = CV_0 e^{-t/RC}$$

also  $i = \frac{V_0}{R} e^{-t/RC}$

a bit about exponential decay:

$$\frac{q}{Q_0} = e^{-t/RC}$$

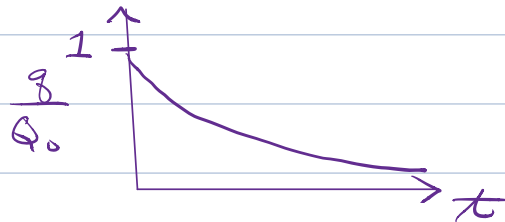

$t$	$q/Q_0$
0	1
1 · RC	$e^{-1} = 1/e = 0.368$
2 · RC	$e^{-2} = 0.135$
3 · RC	$e^{-3} \approx 0.0498$ (~5%)
5 · RC	$e^{-5} \approx 0.0067$ (< 1%)
⋮	⋮

$RC = \text{"time constant"} = \tau$

e.g.  $R = 10 \text{ k}\Omega$   $C = 0.01 \text{ mF} = 10^{-5} \text{ F}$

$$\tau = RC = 10^4 \Omega \cdot 10^{-5} \text{ F} = 10^{-1} \text{ s} = 0.1 \text{ s}$$

e.g.  $R = 500 \text{ k}\Omega$   $C = 5 \mu\text{F}$

$$\tau = RC = 500 \times 10^3 \Omega \cdot 5 \times 10^{-6} \text{ F} = 2.5 \text{ s}$$

RC circuits are widely used for timing.

Question: how long does it take to discharge?  
There is no exact answer. It depends on your precise criteria. After  $\sim 3\tau$ , 95% is gone. After  $\sim 5\tau$ , >99% is gone.

Another description: half life. How long does it take to go down to half of what you have (e.g.  $6V \rightarrow 3V$ , or  $4V \rightarrow 2V$ , etc.)

$$q = Q_0 e^{-t/\tau}$$

$$CV = C V_0 e^{-t/\tau}$$

$$\frac{1}{2} V_0 = V_0 e^{-t/\tau}$$

$$\frac{1}{2} = e^{-t/\tau}$$

$$\ln(1/2) = -t/\tau$$


$$\ln 2 = t/\tau$$

$$t_{1/2} = \tau \ln 2$$

, where

$$\ln 2 \approx 0.693$$

Charging: same shape, but upside down.

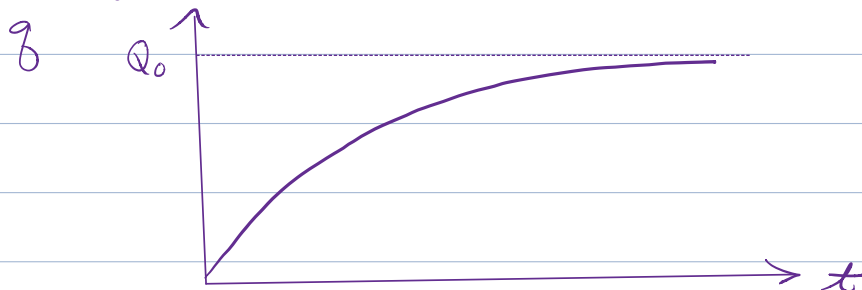

$$q = Q_0 (1 - e^{-t/RC})$$

Not on test

