
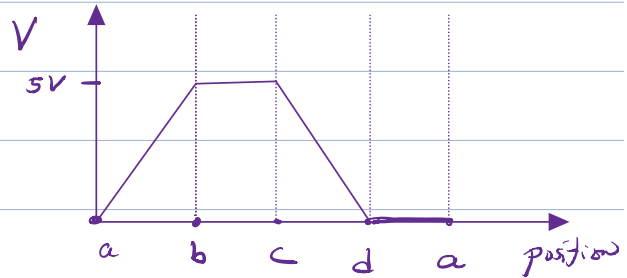


22.3 Batteries and emf

(review)

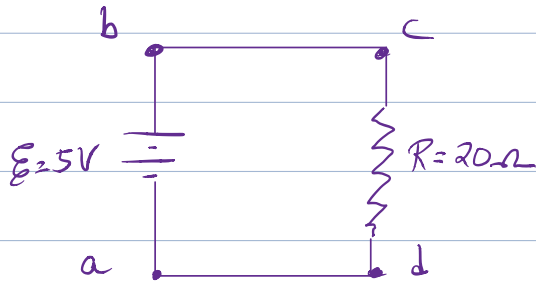

Look at resistor and apply Ohm's Law

$$\Delta V = IR$$

$$5V = I(20\Omega)$$

$$I = \frac{5V}{20\Omega} = 0.25A$$

22.6 energy and power

In 1 second, how much energy did the battery supply? $\Delta U = q_0 \cdot \Delta V$

$$\Delta V = 5V = 5 \text{ J/C}$$

$$q_0 = I \cdot \Delta t$$

$$q_0 = 0.25 \text{ C/s} \cdot 1 \text{ s} = 0.25 \text{ C}$$

$$\Delta U = (0.25 \text{ C})(5 \text{ J/C}) = 1.25 \text{ J}$$

What is the power - the rate at which the battery supplied energy?

$$P = \frac{\Delta U}{\Delta t} = \frac{I \cdot \Delta t \cdot \Delta V}{\Delta t} = I \cdot \Delta V$$

$$P = \left(0.25 \frac{\text{C}}{\text{s}}\right) \cdot \left(5 \frac{\text{J}}{\text{C}}\right) = 1.25 \frac{\text{J}}{\text{s}} = 1.25 \text{ W.}$$

General Rule: $P = I \cdot \Delta V$

What happened to that energy? It was dissipated in the resistor

$$P = I \cdot (-5V) = -1.25 \text{ W}$$

This is called Joule Heating.

Alternate forms for a resistor:
Use Ohm's Law $\Delta V = IR$, or $I = \Delta V/R$

$$P = I \cdot (\Delta V) = I \cdot (IR) = I^2 R = \\ = \left(\frac{\Delta V}{R}\right)^2 \cdot R = \frac{(\Delta V)^2}{R}$$

$$P = I(\Delta V) = I^2 R = \frac{(\Delta V)^2}{R}$$

But the general rule is

$$P = I(\Delta V)$$

electrical safety: at a household 120V outlet
capable of supplying 20A


$$P_{\max} = (20A)(120V) = 2400W - \text{a lot!}$$

e.g. Toaster Oven $P = 1,000W$

$$\mathcal{E} = \Delta V = 110V$$

$$R = ?$$

$$I = ?$$

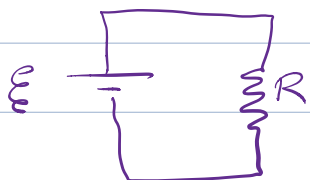

$$P = \mathcal{E}I \Rightarrow I = \frac{P}{\mathcal{E}} = \frac{1000W}{110V} = 9.09A$$

$$R = \frac{\Delta V}{I} = \frac{\mathcal{E}}{I} = \frac{110V}{9.09A} = 12.1\Omega$$

Power supplied by outlet:

$$P = \mathcal{E}I = (110\text{V})(9.09\text{A}) = 1,000\text{ W}$$

Power dissipated by toaster

$$P = I^2R = (9.09\text{A})^2(12.1\Omega) = 1,000\text{ W}$$

Example: Ch 22 - nichrome-wire - pdf.