

### 23.1 Circuit Elements and Diagrams

Read, and watch the pre-lecture video. We will encounter these issues as we discuss specific circuits.

### 23.2 Kirchhoff's Laws


Kirchhoff's Voltage Law (KVL): The sum of voltage drops around a closed loop = 0. This is really a conservation of energy statement. When a charge completes a loop around a circuit, it ends up back where it started.

Kirchhoff's Current Law (KCL): The sum of currents into a junction = the sum of currents leaving a junction. This is really a statement of conservation of charge. There is no build-up of charge at a junction.

These are best illustrated through applications.

### 23.3 Series and Parallel

Start with a simple circuit

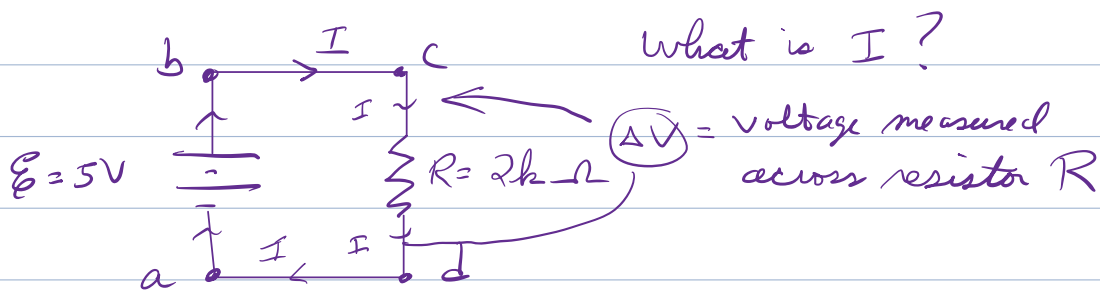

$$\text{KVL: } a \rightarrow b \rightarrow c \rightarrow d \rightarrow a = 0 \text{ Volts}$$

$$+ \underset{\substack{\uparrow \\ \text{gain in battery}}}{\mathcal{E}} + 0 - \underset{\substack{\uparrow \\ \text{loss in resistor}}}{\Delta V} + 0 = 0$$

$$\Delta V = \mathcal{E} = 5 \text{ V}$$

Apply Ohm's Law to the resistor

$$\Delta V = IR$$

$$I = \frac{\Delta V}{R} = \frac{5.0 \text{ V}}{2 \text{ k}\Omega} = 2.5 \text{ mA}$$

$I$  is the same everywhere in this circuit.

Note on units:

$$1 \text{ k}\Omega = 10^3 \Omega$$

$$1 \text{ mA} = 10^{-3} \text{ A}$$

$$(1 \text{ k}\Omega)(1 \text{ mA}) = 10^3 \Omega \cdot 10^{-3} \text{ A} = \\ = 1 \Omega \cdot \text{A} = 1 \text{ V}$$

Power considerations:

Power supplied by the battery

$$P_{\mathcal{E}} = I\mathcal{E} = (2.5 \text{ mA})(5 \text{ V}) = 12.5 \text{ mW}$$


Power dissipated by the resistor

$$P_R = I^2 R = (2.5 \text{ mA})^2 (2 \text{ k}\Omega) = 12.5 \text{ mW}$$

They match!
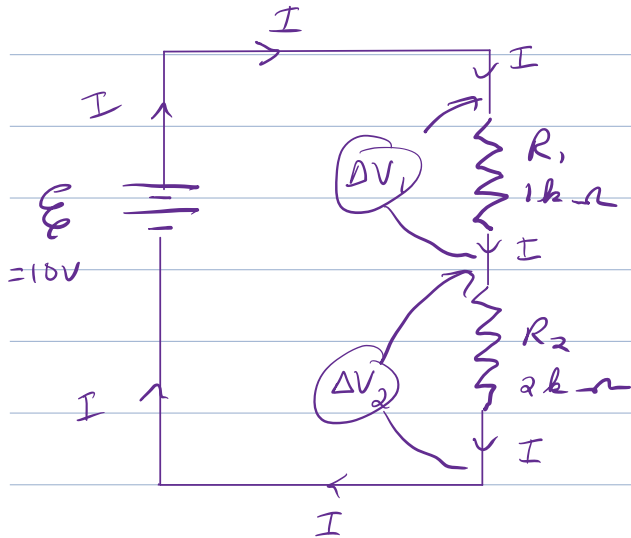
## Series Example

$$\mathcal{E} = 10V \quad R_1 = 1k\Omega \quad R_2 = 2k\Omega$$



Series: Same current goes through first one then the other

Question: what is  $I$ ?  
(Poll on  $I$  &  $V$ .)

$$\text{KVL} \quad \mathcal{E} - \Delta V_1 - \Delta V_2 = 0$$


$$\mathcal{E} - IR_1 - IR_2 = 0$$

$$\mathcal{E} = I(R_1 + R_2)$$

$$I = \frac{\mathcal{E}}{(R_1 + R_2)} = \frac{10V}{1k\Omega + 2k\Omega} = 3.33mA$$

Series equivalent: As far as the battery is concerned, this series combination acts as if the series were replaced by a single resistor

$$R_S = R_1 + R_2 = 3k\Omega$$

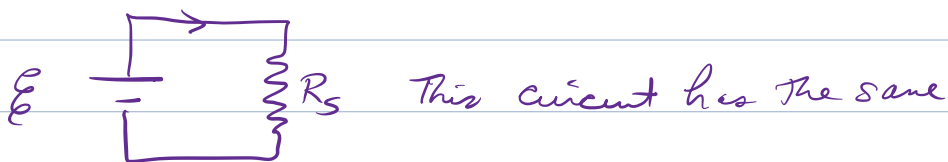

Generalized Series equivalent:  $R_1$   $R_2$   $R_3$

$$R_s = R_1 + R_2 + R_3 + \dots$$


Go back and label voltages:

$$\Delta V_1 = IR_1 = (3.33\text{mA})(1\text{k}\Omega) = 3.33\text{V}$$

$$\Delta V_2 = IR_2 = (3.33\text{mA})(2\text{k}\Omega) = 6.67\text{V}$$

$$\text{add: } \Delta V_1 + \Delta V_2 = 10\text{V} \quad \checkmark$$

also - label in diagram.

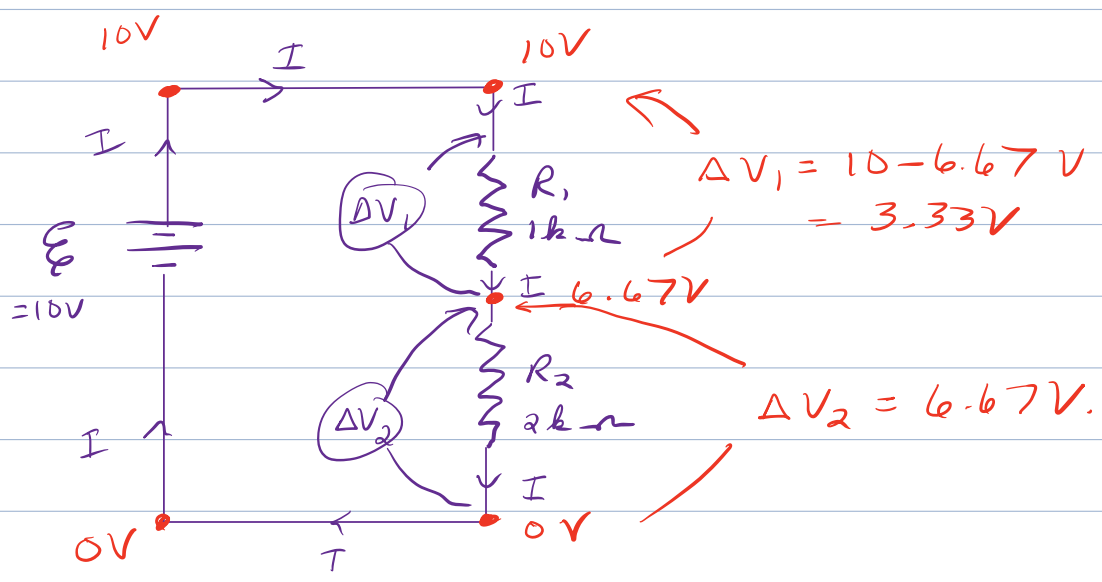

## Power considerations

$$\text{Battery: } P_{\xi} = \xi I = (10\text{V})(3.33\text{mA}) = 33.3\text{mW}$$

Resistor 1:

$$P_1 = I^2 R_1 = (3.33\text{mA})^2 (1\text{k}\Omega) = 11.1\text{mW}$$

$$\text{(OR: } P_1 = I \Delta V_1 = (3.33\text{mA})(3.33\text{V}) = 11.1\text{mW} \text{)}$$


Resistor 2:

$$P_2 = I^2 R_2 = (3.33\text{mA})^2 (2\text{k}\Omega) = 22.2\text{mW}$$

$$\text{(OR: } P_2 = I \Delta V_2 = (3.33\text{mA})(6.67\text{V}) = 22.2\text{mW} \text{)}$$

$$\text{Total } P_1 + P_2 = 11.1\text{mW} + 22.2\text{mW} = 33.3\text{mW} \checkmark$$

## Parallel example

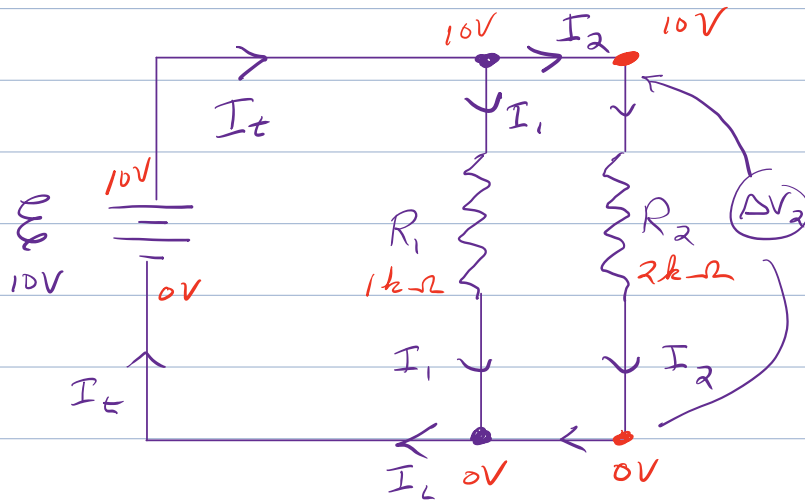

$$\mathcal{E} = 10\text{V}$$

$$R_1 = 1\text{k}\Omega$$

$$R_2 = 2\text{k}\Omega$$

Parallel:

current goes

through one or the

other, but not both.

Question: what is  $I_t$ ? (Poll on I & V)

KCL: at a junction:  $I_t = I_1 + I_2$ .

What are  $I_1$  and  $I_2$ ? Use Ohm's Law


$$I_1 = \frac{\Delta V_1}{R_1} = \frac{\mathcal{E}}{R_1} = \frac{10\text{V}}{1\text{k}\Omega} = 10\text{mA}$$

$$1\text{mA} \cdot 1\text{k}\Omega = 1\text{V}$$

$$I_2 = \frac{\Delta V_2}{R_2} = \frac{\mathcal{E}}{R_2} = \frac{10\text{V}}{2\text{k}\Omega} = 5\text{mA}$$

$$I_t = I_1 + I_2 = 10\text{mA} + 5\text{mA} = 15\text{mA}$$

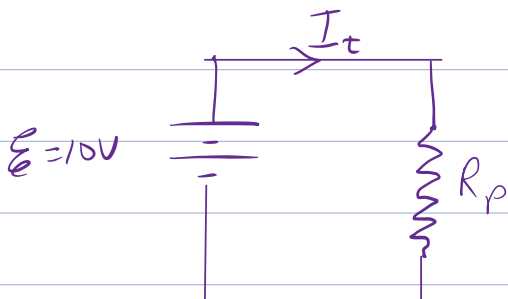From the perspective of the battery, this is equivalent to a single resistor  $R_p$



$$I_t = \frac{\mathcal{E}}{R_p} \Rightarrow R_p = \frac{\mathcal{E}}{I_t}$$

$$R_p = \frac{10\text{V}}{15\text{mA}} = 0.667\text{k}\Omega$$

Symbolically: Use KCL


$$I_t = I_1 + I_2$$

$$\frac{E}{R_p} = \frac{E}{R_1} + \frac{E}{R_2}$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_p = \frac{R_1 R_2}{R_1 + R_2}$$

### Generalized parallel resistance

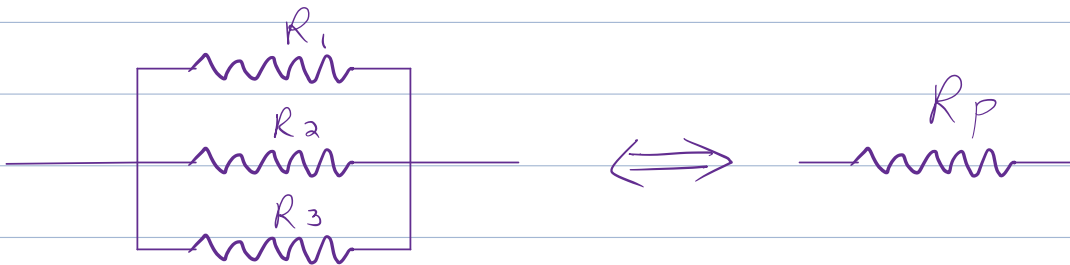

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$


e.g here  $\frac{1}{R_p} = \frac{1}{1k\Omega} + \frac{1}{2k\Omega} = \frac{2+1}{2k\Omega} = \frac{3}{2k\Omega}$

$$R_p = \frac{2}{3} k\Omega = 0.667 k\Omega$$

handy parallel trick: if  $R_1 = R_2 = R$ ,  $R_p = \frac{1}{2} R$ .

$R_s >$  (all the  $R$ 's)

$R_p <$  (all the  $R$ 's)

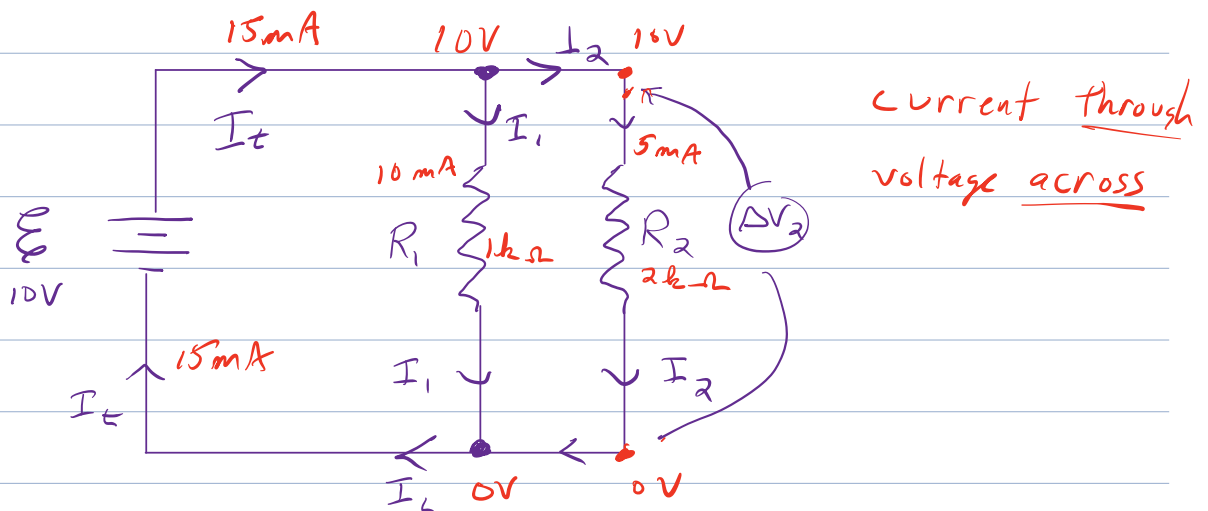

Power considerations

$$\text{Battery: } P_{\xi} = \xi I = (10\text{V})(15\text{mA}) = 150\text{mW}$$

$$R_1: P_1 = I_1 (\Delta V_1) = I_1^2 R_1 = (10\text{mA})^2 (1\text{k}\Omega) = 100\text{mW}$$

$$R_2: P_2 = I_2 (\Delta V_2) = I_2^2 R_2 = (5\text{mA})^2 (2\text{k}\Omega) = 50\text{mW}$$

$$P_1 + P_2 = 100\text{mW} + 50\text{mW} = 150\text{mW} \quad \checkmark$$

Next: combinations. Sometimes can replace combinations by simpler series or parallel equivalents.