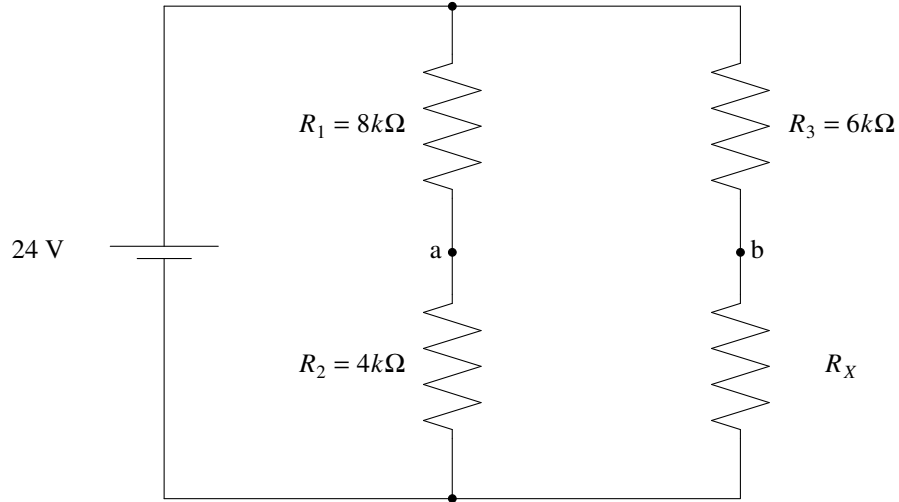



Problem 2: (30 pts.) Consider the circuit below, known as a Wheatstone Bridge.



- a. (15 pts.) If the voltage difference V_{ab} is measured to be 0 V, what is the unknown resistance R_X ?

- b. (15 pts.) Next, resistor R_X is replaced by a new unknown resistor R_Y . The voltage $V_{ab} = V_a - V_b$ is now measured to be 2.00 V. What is R_Y ? (In this type of circuit, measurements of V_{ab} can be used to monitor changes in resistance of R_Y .)

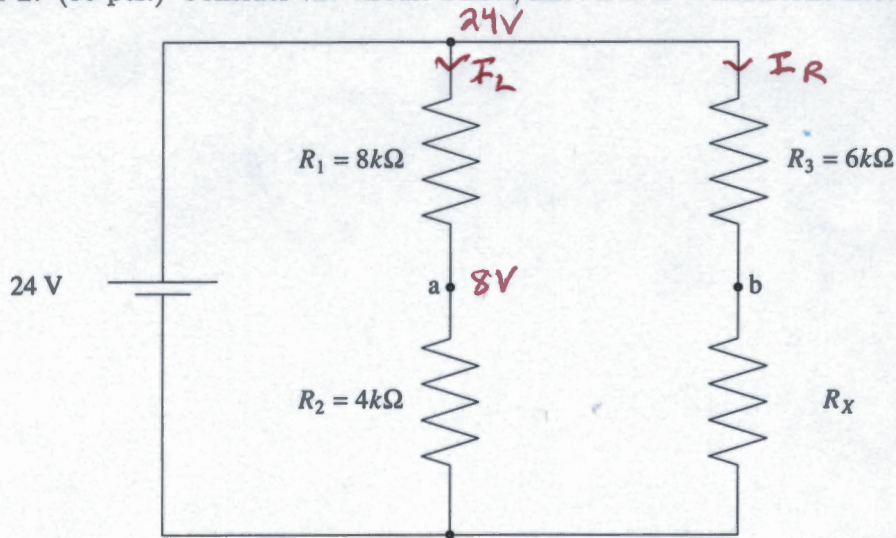Problem 2: (30 pts.) Consider the circuit below, known as a Wheatstone Bridge.



- a. (15 pts.) If the voltage difference V_{ab} is measured to be 0 V, what is the unknown resistance R_X ?

$$I_L = \frac{24V}{8k\Omega + 4k\Omega} = 2mA$$

$$V_a = I_L R_2 = 8V$$

$$V_1 = \text{voltage across resistor 1} = I_L R_1 = 16V$$

$$\therefore \text{Require } V_b = 8V \rightarrow V_2 = 16V, \text{ so } I_R = \frac{16V}{6k\Omega}$$

$$\text{Lastly, require } V_b = 8V = I_R R_X \Rightarrow R_X = \frac{8V}{16V/6k\Omega} = \boxed{3k\Omega}$$

- b. (15 pts.) Next, resistor R_X is replaced by a new unknown resistor R_Y . The voltage $V_{ab} = V_a - V_b$ is now measured to be 2.00 V. What is R_Y ? (In this type of circuit, measurements of V_{ab} can be used to monitor changes in resistance of R_Y .)

$$\text{Now, require } V_b = 6V, \text{ so } I_R = \frac{24-6}{6k\Omega} = 3mA$$

$$\text{Then, since } V_b = 6V = I_R R_Y, \quad R_Y = \frac{6V}{3mA} = \boxed{2k\Omega}$$