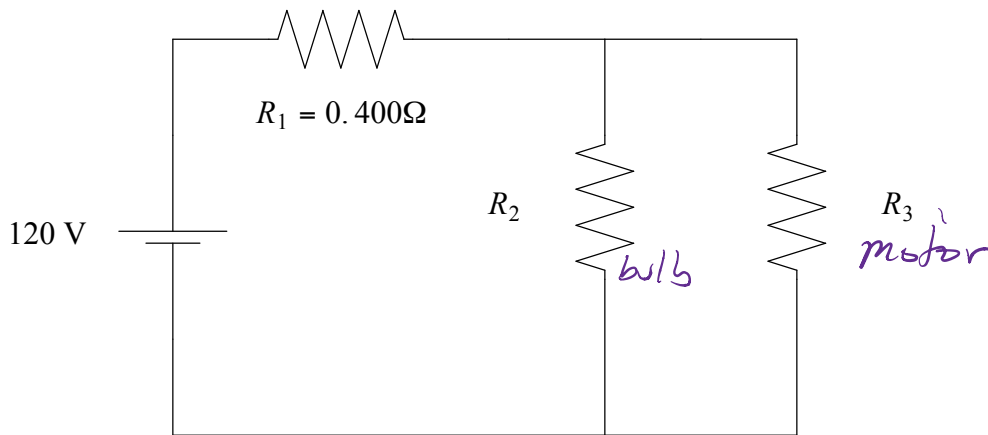



Physics 133
Sample Test Problem

Problem 1. (30 pts.) When a powerful appliance switches on, the lights on the same circuit often dim noticeably. In this problem, you will calculate this effect for the following idealized simplified circuit. Resistance R_1 represents the total resistance in the wires and connections, R_2 is a light bulb, and R_3 is a motor. (For the purposes of this problem, assume that all these resistances are fixed, constant values.)



- (15 pts.) When the motor is off (or disconnected), a total current of 0.626 A passes through R_1 . What is the power dissipated by the light bulb?
- (5 pts.) When the motor is on, a total current of 30.0 A passes through R_1 . What is the voltage across R_1 ?
- (10 pts.) When the motor is on, what is the power dissipated by the light bulb?

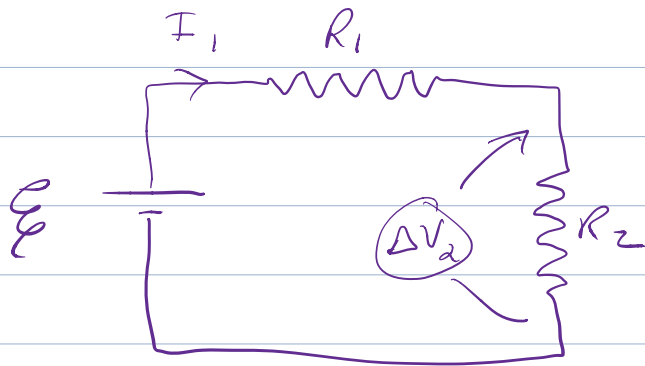(a) Redraw the circuit with the motor disconnected



$$\mathcal{E} = 120\text{V}$$

$$R_1 = 0.400\ \Omega$$

$$R_2 = ?$$

$$I_1 = 0.626\text{A}$$

Since R_1 and R_2 are in series,

$$I_1 = \frac{\mathcal{E}}{R_1 + R_2} \Rightarrow R_1 + R_2 = \frac{\mathcal{E}}{I_1}$$

$$R_2 = \frac{\mathcal{E}}{I_1} - R_1 = \frac{120\text{V}}{0.626\text{A}} - 0.400\ \Omega \approx 191.3\ \Omega$$

To calculate P_2 (how "bright" is the bulb?) we can use $P_2 = I_2(\Delta V_2)$ or $I_2^2 R_2$.
What is ΔV_2 ?


$$\Delta V_2 = I_2 R_2 = I_1 R_2 = 119.75\text{V}$$

$$\text{note: } \Delta V_1 = I_1 R_1 = 0.25\text{V}$$

$$\text{Then } P_2 = I_2 \Delta V_2 = (0.626\text{A})(119.75\text{V})$$

$$P_2 = 75\text{W}$$

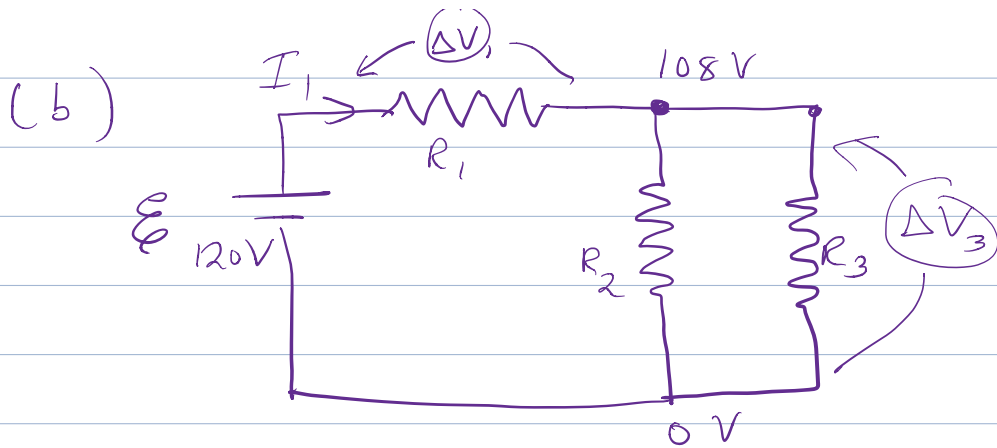Now that we know R_2 (bulb) return to the full circuit



$$\mathcal{E} = 120\text{V}$$

$$R_1 = 0.400\ \Omega$$

$$I_1 = 30.0\ \text{A}$$

$$\Delta V_1 = I_1 R_1 = (30.0\ \text{A})(0.400\ \Omega)$$

$$\Delta V_1 = 12.0\ \text{V}$$

$$R_2 = 191.3\ \Omega$$

$$R_3 = ?$$

(c) What is P_2 ?

$$P_2 = I_2 (\Delta V_2) = \left(\frac{\Delta V_2}{R_2}\right) (\Delta V_2) = \frac{(\Delta V_2)^2}{R_2}$$

What is ΔV_2 ?

$$\mathcal{E} \text{ is } 120\ \text{V}$$

$$\Delta V_1 \text{ is } 12\ \text{V}$$

$$\therefore \Delta V_2 \text{ is } 108\ \text{V}$$

KVL:

$$\mathcal{E} - \Delta V_1 - \Delta V_2 = 0$$


$$\Delta V_2 = \mathcal{E} - \Delta V_1$$

$$= 120\ \text{V} - 12\ \text{V}$$


$$\Delta V_2 = 108\ \text{V}$$

$$P_2 = \frac{(108\ \text{V})^2}{191.3\ \Omega} = \boxed{61.0\ \text{W}} \text{ The bulb dims.}$$

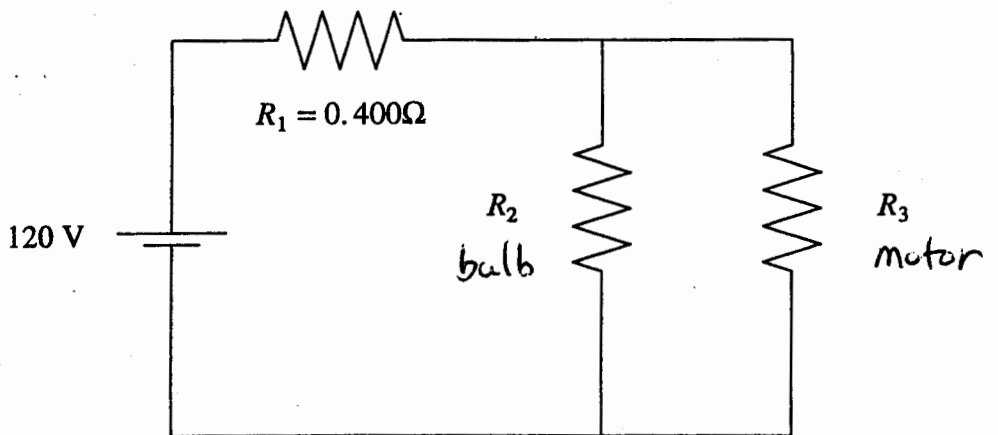4. (30 pts.) When a powerful appliance switches on, the lights on the same circuit often dim noticeably. In this problem, you will calculate this effect for the following idealized simplified circuit. Resistance R_1 represents the total resistance in the wires, R_2 is a light bulb, and R_3 is a motor. (For the purposes of this problem, assume that all these resistances are fixed, constant values.)



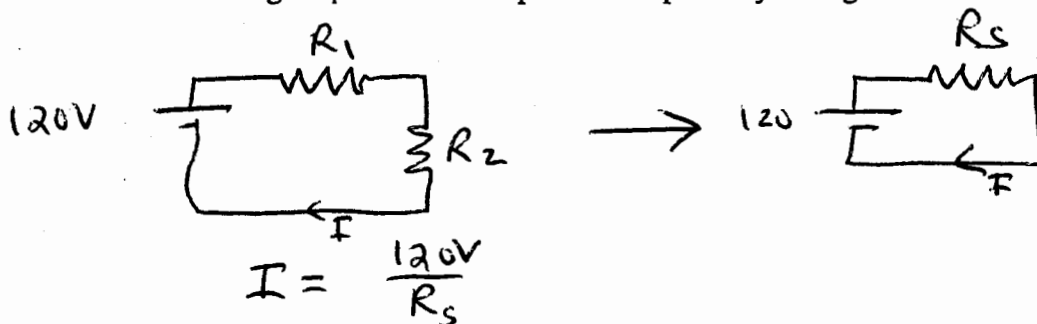- a. (15 pts.) When the motor is off (or disconnected), a total current of 0.626 A passes through R_1 . What is the power dissipated by the light bulb?



$$0.626 \text{ A} = \frac{120 \text{ V}}{R_s} \Rightarrow R_s = \frac{120 \text{ V}}{0.626 \text{ A}} = 191.7 \Omega$$

$$\text{Now } R_s = R_1 + R_2 \Rightarrow R_2 = R_s - R_1 = 191.7 - 0.4$$

$$R_2 = 191.3 \Omega$$

$$\text{Lastly } P_2 = \cancel{I^2 R_2} = V_2 I_2 = (I_2 R_2) I_2 = I_2^2 R_2$$

$$P_2 = (0.626)^2 (191.3) = \boxed{75.0 \text{ W}}$$

- b. (5 pts.) When the motor is on, a total current of 30.0 A passes through R_1 . What is the voltage across R_1 ?

$$V_1 = I_1 R_1 = (30\text{A})(0.400\ \Omega) = 12\text{V}$$

- c. (10 pts.) When the motor is on, what is the power dissipated by the light bulb?

$$P_2 = V_2 I_2 = V_2 \left(\frac{V_2}{R_2} \right) = \frac{V_2^2}{R_2}$$

$$V_2 = 120\text{V} - 12\text{V} \quad (\text{KVL}) = 108\text{V}$$

$$P_2 = \frac{(108)^2}{191.3} = \boxed{61.0\text{W}}$$