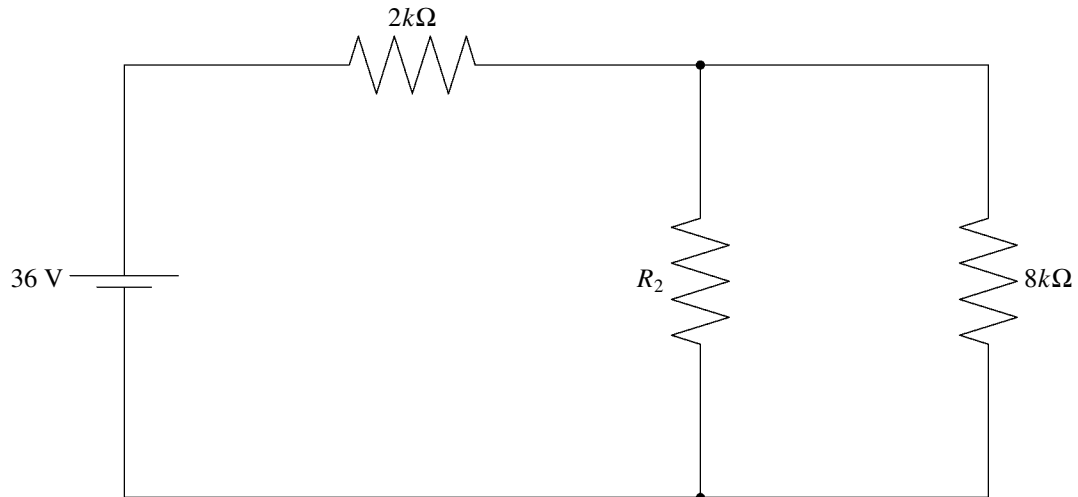


Problem 3: (30 pts.) In the circuit shown in the figure, energy is being dissipated in the $8.00\text{ k}\Omega$ resistor at a rate of 80.7 mW .


a. (25 pts.) What is the resistance R_2 ?



b. (5 pts.) Now suppose R_2 were doubled. Would the power in the $8\text{ k}\Omega$ resistor increase, decrease, or stay the same? Explain your answer briefly, but clearly.

Problem 3: (30 pts.) In the circuit shown in the figure, energy is being dissipated in the $8.00 \text{ k}\Omega$ resistor at a rate of 80.7 mW .

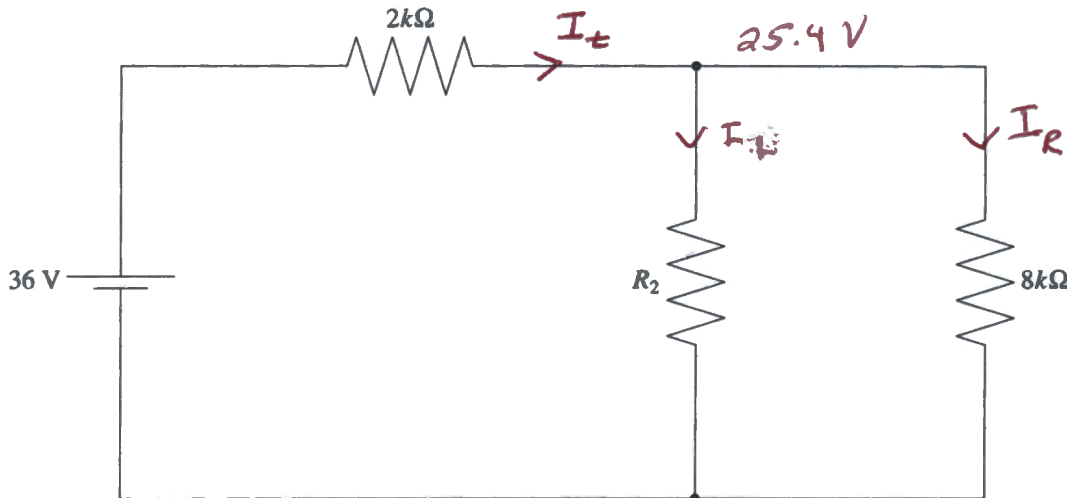a. (25 pts.) What is the resistance R_2 ?



$$P_R = 80.7 \text{ mW} = I_R^2 (8 \text{ k}\Omega) \Rightarrow I_R = 3.176 \text{ mA}$$

$$\text{Then } V_R = I_R (8 \text{ k}\Omega) = 25.41 \text{ V}$$

$$\text{Then } I_t = \frac{36 - 25.4}{2 \text{ k}\Omega} = 5.30 \text{ mA}$$

$$\text{Next, } I_L = I_t - I_R = 2.12 \text{ mA}$$

$$\text{Finally, } 25.4 \text{ V} = I_L R_2 \Rightarrow R_2 = \frac{25.4 \text{ V}}{2.12 \text{ mA}} = \boxed{12.0 \text{ k}\Omega}$$

b. (5 pts.) Now suppose R_2 were doubled. Would the power in the $8 \text{ k}\Omega$ resistor increase, decrease, or stay the same? Explain your answer briefly, but clearly.

Increase. If R_2 doubles, less current is drawn. (The equivalent parallel resistance of R_2 and $8 \text{ k}\Omega$ increases). Less current in total means the voltage drop V_1 over the $2 \text{ k}\Omega$ resistor is less. Thus the voltage across the $8 \text{ k}\Omega$ resistor is now more than 25.4 V , and the power, V^2/R , increases.