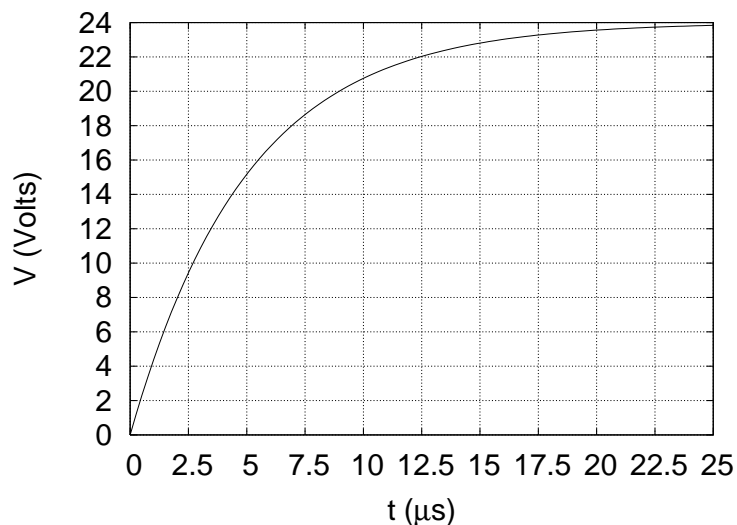


3. (20 pts.) A 24V battery with negligible internal resistance is connected in series with a  $40\text{ k}\Omega$  resistor, an unknown inductor, and an open switch. The switch is closed at time  $t = 0$ . The voltage as a function of time across one of the circuit elements is shown in the following figure. (Note that the horizontal scale is in microseconds.)



- a. (5 pts.) Across which circuit element is the voltage in the figure being measured? Explain your reasoning. No credit will be given for an answer without correct reasoning.
- b. (15 pts.) What is the inductance of the inductor? You may assume the internal resistance of the inductor is zero. (Recall that  $t_{1/2} = \tau \ln 2$ .)