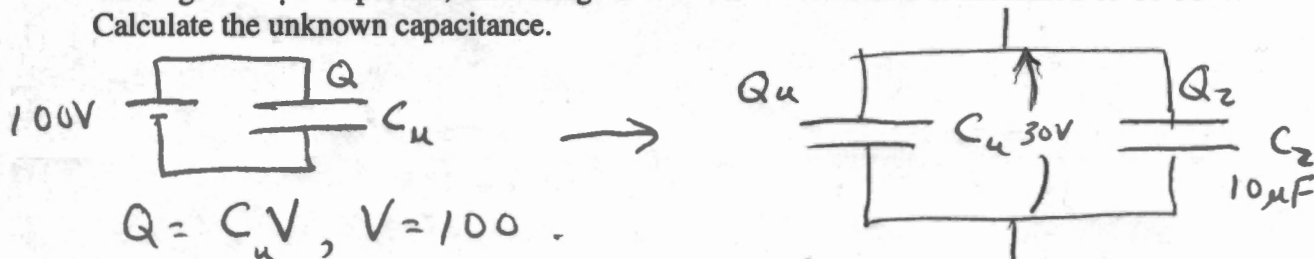


5. (10 pts.) An isolated capacitor of unknown capacitance has been charged to a potential difference of 100 V. When the charged capacitor is then connected in parallel to an uncharged  $10\ \mu\text{F}$  capacitor, the voltage across the combination is measured to be 30 V. Calculate the unknown capacitance.

5. (10 pts.) An isolated capacitor of unknown capacitance has been charged to a potential difference of 100 V. When the charged capacitor is then connected in parallel to an uncharged  $10 \mu\text{F}$  capacitor, the voltage across the combination is measured to be 30 V. Calculate the unknown capacitance.



$$Q = C_u V, V = 100.$$

$C_u =$  unknown capacitance.

total charge  $Q$  splits into two:  $Q = Q_u + Q_2$

$$C_2 = 10 \mu\text{F}$$

$$V = 30\text{V}.$$

Now use conservation of charge and  $Q = CV$ .

$$Q = Q_u + Q_2$$

$$(C_u)(100) = (C_u)(30\text{V}) + (10 \mu\text{F})(30\text{V})$$

$$70 C_u = 300 \mu\text{C}$$

$$C_u = 4.29 \mu\text{F}$$