


30.23

- A 35.0 V battery with negligible internal resistance, a 50.0 Ω resistor, and a 1.25 mH inductor with negligible resistance are all connected in series with an open switch. The switch is suddenly closed. (a) How long after closing the switch will the current through the inductor reach one-half of its maximum value? (b) How long after closing the switch will the energy stored in the inductor reach one-half of its maximum value?

Phys 132

HW #9

30.21

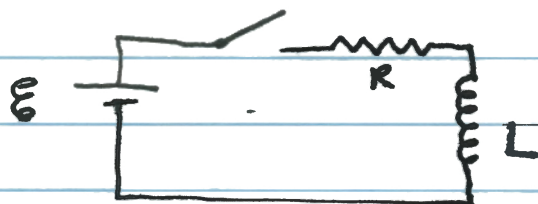

$$\mathcal{E} = 35\text{V}$$

$$R = 50\ \Omega$$

$$L = 1.25\text{mH}$$

A. $\tau = L/R = 2.5 \times 10^{-5}\text{ s}$
 $t_{1/2} = \tau \ln 2 = 1.73 \times 10^{-5}\text{ s}$

B. $U = \frac{1}{2} L i^2$ $i = i_0 (1 - e^{-t/\tau})$

$$U_0 = \frac{1}{2} L i_0^2$$

when i_0 $U = \frac{1}{2} U_0$

$$\frac{1}{2} L i^2 = \frac{1}{2} \left[\frac{1}{2} L i_0^2 \right]$$

$$i^2 = \frac{1}{2} i_0^2$$

$$i_0^2 (1 - e^{-t/\tau})^2 = \frac{1}{2} i_0^2$$

$$1 - e^{-t/\tau} = 1/\sqrt{2}$$

$$e^{-t/\tau} = 1 - 1/\sqrt{2}$$

$$\ln e^{-t/\tau} = \ln(1 - 1/\sqrt{2})$$

$$-t/\tau = \ln(1 - 1/\sqrt{2})$$

$$t = -\tau \ln(1 - 1/\sqrt{2}) = - (2.5 \times 10^{-5}\text{ s}) (-1.2279)$$

$$\boxed{t = 3.07 \times 10^{-5}\text{ s}}$$

30.32

$$C = 3.23\ \mu\text{F} \quad L = 89\ \text{mH}$$

$$i_{\text{max}} = 0.849\ \text{mA}$$

A consider energy: $U_L = \frac{1}{2} L i^2$ $U_C = \frac{1}{2} C Q^2$

$$\therefore \frac{1}{2} L i_{\text{max}}^2 = \frac{1}{2} C q_{\text{max}}^2$$

$$q_{\text{max}} = \sqrt{LC} i_{\text{max}} = \boxed{4.55 \times 10^{-4}\ \text{C}}$$