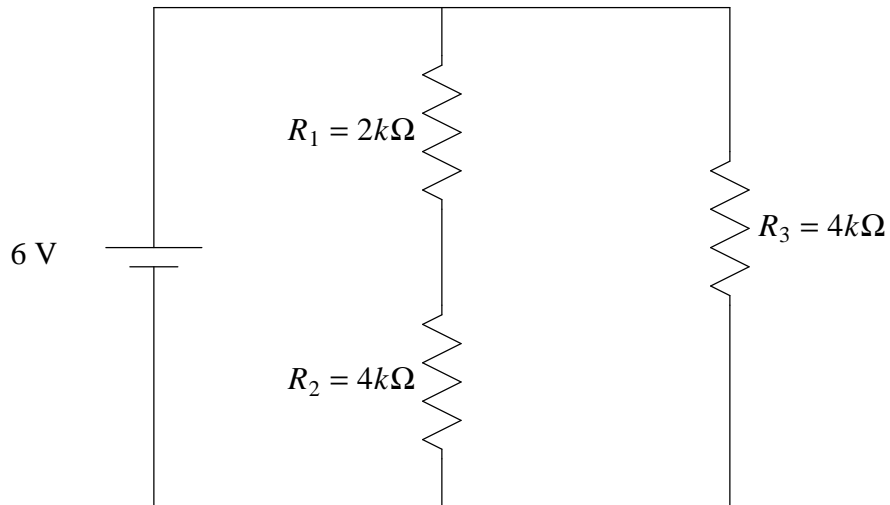



2. (30 pts.) Consider the following circuit.



a. (15 pts.) Find the total power delivered by the battery.


b. (15 pts.) Find the power dissipated in resistor R_2 .

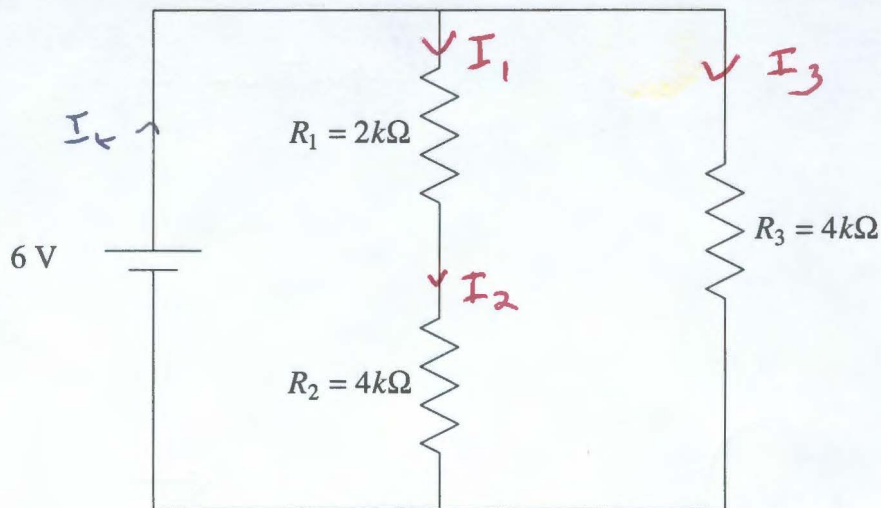2. (30 pts.) Consider the following circuit.



a. (15 pts.) Find the total power delivered by the battery.

Equivalent circuits:

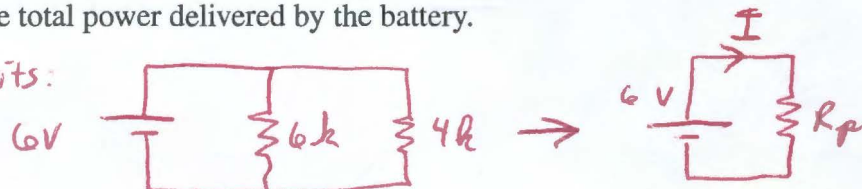

$$\frac{1}{R_p} = \frac{1}{6k} + \frac{1}{4k} = \frac{5}{12k} \Rightarrow R_p = \frac{12}{5}k = 2.4k\Omega$$

$$I = \frac{6V}{2.4k\Omega} = 2.5mA$$

$$P = \mathcal{E} I = (6V)(2.5mA) = \boxed{15mW}$$

b. (15 pts.) Find the power dissipated in resistor R_2 .

Here's one way: $I_1 = \frac{6V}{2k + 4k} = 1mA$

$$I_1 = I_2$$

$$P_2 = I_2^2 R_2 = (1mA)^2 (4k\Omega) = \boxed{4mW}$$