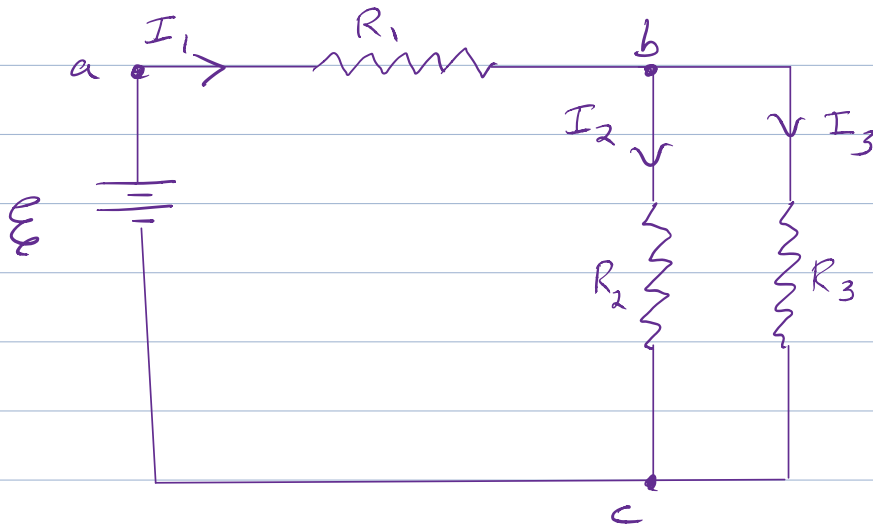


## 23.5 More Complex Circuits

Start with an example:



$$\mathcal{E} = 10 \text{ V} \quad R_1 = 1 \text{ k}\Omega \quad R_2 = 2 \text{ k}\Omega \quad R_3 = 3 \text{ k}\Omega$$

Problem: Find  $I_1$ ,  $I_2$ , and  $I_3$ .

(Poll-combinations)

How to start? we would like to use


$$P = I (\Delta V) \quad \text{or} \quad \Delta V = IR, \quad \text{but we}$$

don't know any of the currents or voltage drops.

Plan: try to replace some resistors by series or parallel equivalents till we can figure out some of the currents or voltages.

Note:  $R_2$  and  $R_3$  are in parallel.

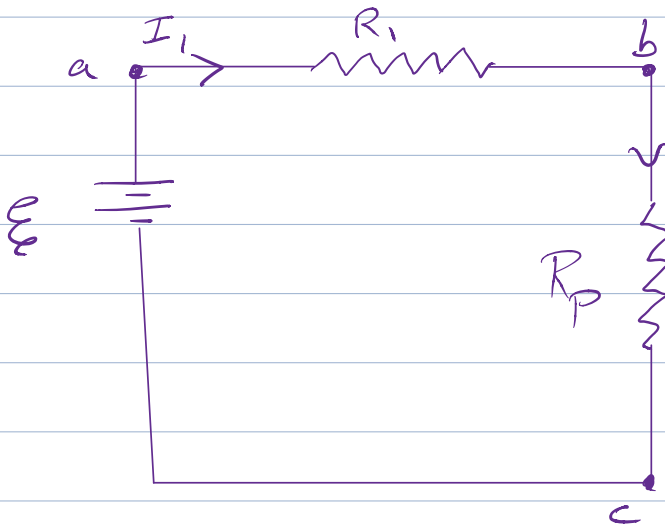Replace them by  $R_p$  on the way to finding the current delivered by the battery.




$$\frac{1}{R_p} = \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{2k\Omega} + \frac{1}{3k\Omega} = \frac{5}{6k\Omega}$$

$$R_p = \frac{6k\Omega}{5} = 1.2k\Omega$$

Next: Note  $R_1$  and  $R_p$  are in series, so as far as the battery is concerned, replace them by the series equivalent  $R_s = R_1 + R_p$

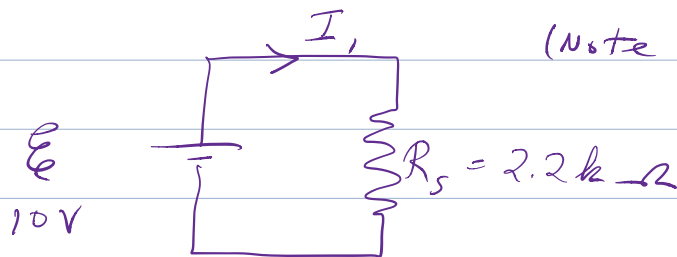
$$R_s = 1k\Omega + 1.2k\Omega = 2.2k\Omega$$



(Note this is still  $I_1$ .)

$$I_1 = \frac{E}{R_s} = \frac{10V}{2.2k\Omega} = 4.55mA$$

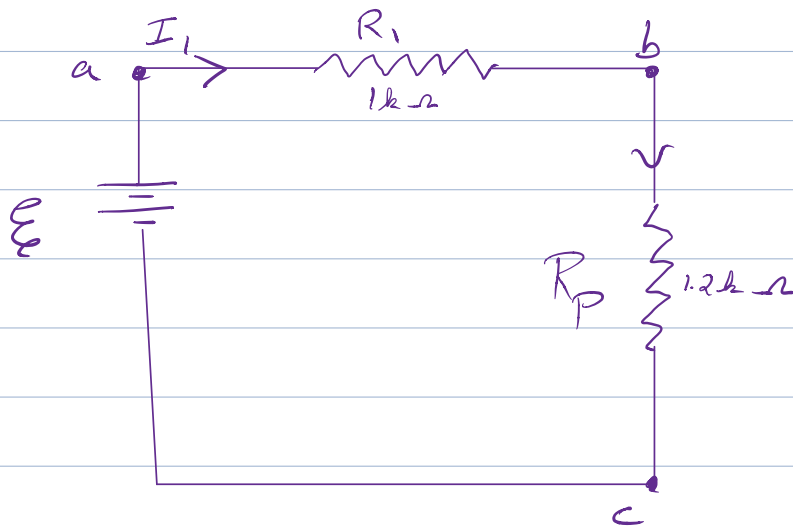Now, start rebuilding the more complex circuit.



Question: what is the voltage at point b?

---


$$\Delta V_1 = I_1 R_1 = (4.55 \text{ mA})(1 \text{ k}\Omega) = 4.55 \text{ V}$$

$$\Delta V_2 = I_1 R_P = (4.55 \text{ mA})(1.2 \text{ k}\Omega) = 5.45 \text{ V}$$

$$\therefore V \text{ at } b = 5.45 \text{ V}$$

$$\text{and } \Delta V_1 = 10 \text{ V} - 5.45 \text{ V} = 4.55 \text{ V} \quad \checkmark$$

Lastly, return to original circuit:

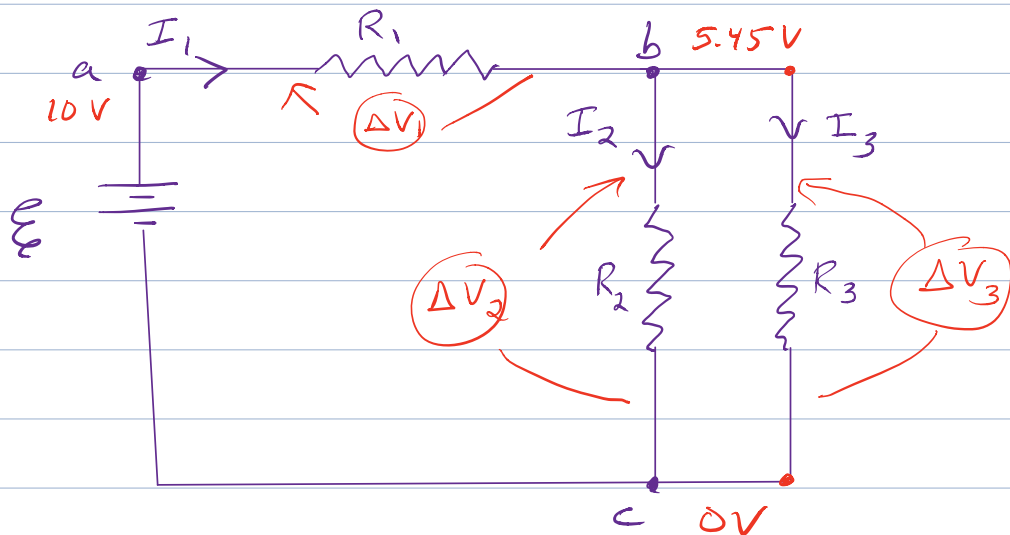

Poll: how do voltages  $\Delta V_2$  and  $\Delta V_3$  compare?  
 how do the currents  $I_2$  and  $I_3$  compare?

look at resistor  $R_2$ :  $\Delta V_2 = I_2 R_2$   

$$I_2 = \frac{\Delta V_2}{R_2} = \frac{5.45V}{2k\Omega} = 2.73mA$$

Look at resistor  $R_3$ :  $\Delta V_3 = I_3 R_3$   

$$I_3 = \frac{\Delta V_3}{R_3} = \frac{5.45V}{3k\Omega} = 1.82mA$$

Note:  $I_1 \stackrel{?}{=} I_2 + I_3$  (KCL)  
 $4.55mA \stackrel{?}{=} 2.73mA + 1.82mA$   
 $4.55mA = 4.55mA \quad \checkmark$

Power considerations: check: is

$$\mathcal{E} I_1 = P_1 + P_2 + P_3 ?$$

$$P_{\mathcal{E}} = \mathcal{E} I_1 = (10V)(4.55mA) = 45.50mW$$

$$P_1 = I_1^2 R_1 = (4.55mA)^2 (1k\Omega) = 20.70mW$$

$$P_2 = I_2^2 R_2 = (2.73mA)^2 (2k\Omega) = 14.91mW$$

$$P_3 = I_3^2 R_3 = (1.82mA)^2 (3k\Omega) = 9.94mW$$

$$\text{total: } 45.55mW$$

These match to within our roundoff error.

See posted examples for chapter 23

Ch 23-combo - 1 } to be discussed  
Ch 23-appliance } in class as  
time permits. (There  
are more examples  
on line -)